

3

# 电路原理习题课



The diagram shows a single-phase AC circuit. On the left, there is a voltage source represented by two open circles with a '+' sign at the top and a '-' sign at the bottom. The voltage is labeled  $u$ . A red arrow labeled  $i$  indicates the current flowing from the positive terminal to the right. The circuit is a single loop containing a load impedance  $Z$ , represented by a blue rectangle. To the right of the rectangle, the impedance is given as  $Z = |Z| \angle \varphi$ .

$$u(t) = 10 \sin(400\pi t + 60^\circ) \text{ V}$$

$$i(t) = -\frac{1}{\sqrt{2}} \cos(400\pi t - 150^\circ) \text{ A}$$


- (a)  $\omega = \underline{400\pi \text{ rad/s}}$ ,  $f = \underline{200\text{Hz}}$ ,  $T = \underline{0.005\text{s}}$ .
- (b) 有效值  $U = \underline{7.07\text{V}}$ , 有效值  $I = \underline{0.5\text{A}}$ .
- (c)  $u$  和  $i$  的相位差  $\psi_u - \psi_i = \underline{-60^\circ}$ .
- (d) 负载是 容性,  $|Z| = \underline{14.14\Omega}$ ,  $\varphi = \underline{-60^\circ}$ .

$$\begin{aligned} i(t) &= \frac{1}{\sqrt{2}} \cos(400\pi t - 150^\circ + 180^\circ) = \frac{1}{\sqrt{2}} \cos(400\pi t + 30^\circ) \\ &= \frac{1}{\sqrt{2}} \sin(400\pi t + 30^\circ + 90^\circ) = \frac{1}{\sqrt{2}} \sin(400\pi t + 120^\circ) A \end{aligned}$$

$$\varphi = \psi_u - \psi_i = 60^\circ - 120^\circ = -60^\circ$$

## 0.2 下列哪些表达式是正确的，哪些是错误的，并改正。

①

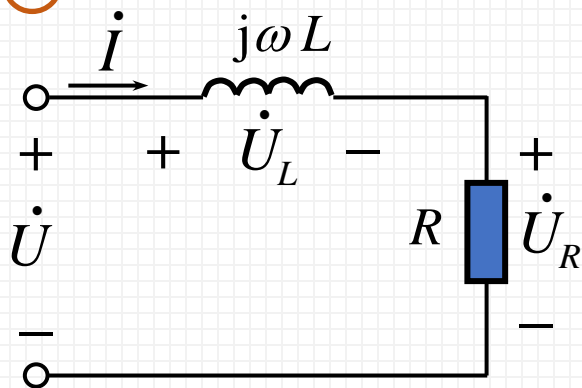

$$(1) \dot{I} = \frac{\dot{U}}{R + j\omega L}$$

$$(2) I = \frac{U}{\sqrt{R^2 + (\omega L)^2}}$$

$$\checkmark (3) u = u_R + u_L$$

$$(4) U^2 = U_L^2 + U_R^2$$

$$\dot{U} = \dot{U}_R + \dot{U}_L$$


$$(5) P = \frac{U_R^2}{R}$$

$$\checkmark (6) P = I^2 R$$

$$(7) |Z| = \sqrt{R^2 + (\omega L)^2}$$

如果  $u(t) = 311\sin(\omega t + 45^\circ)\text{V}$ ,  $Z = 25\angle 60^\circ \Omega$

②

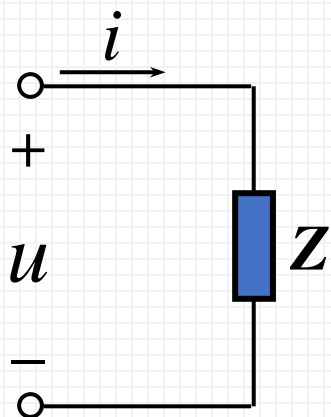


那么  $i \times \frac{u}{Z} \times \frac{311\sin(\omega t + 45^\circ)}{25\angle 60^\circ} \times 12.44\sin(\omega t + 45^\circ - 60^\circ)\text{A}$

$$\dot{I} = \frac{\dot{U}}{Z} = \frac{\frac{311}{\sqrt{2}}\angle 45^\circ}{25\angle 60^\circ} = 8.8\angle -15^\circ \text{ A}$$

相量  $\times$  正弦量

$$i = 8.8\sqrt{2}\sin(\omega t - 15^\circ) \text{ A}$$
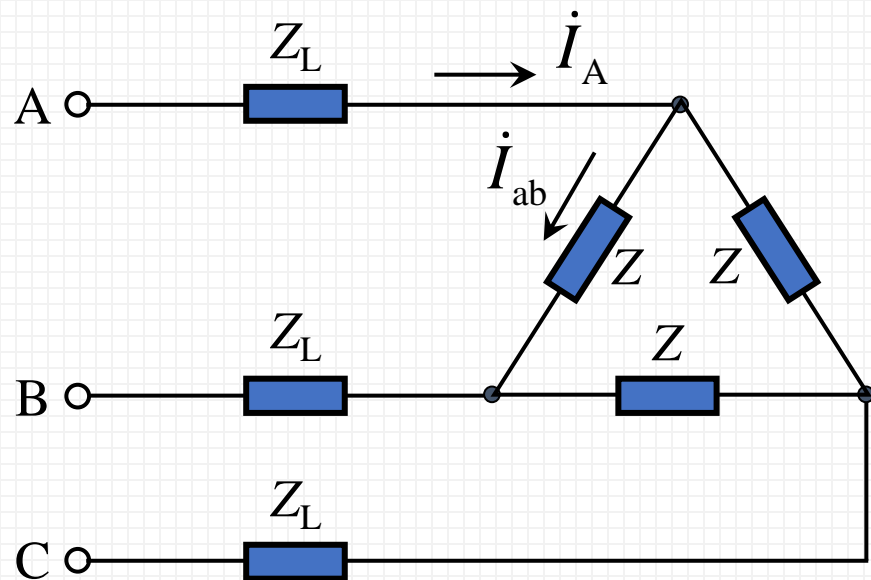
### 0.3 平衡三相电路中, $\dot{U}_{AB}$ 是线电压, $\dot{U}_{AN}$ 是相电压.



(1)  $i_{ab} \neq \frac{\dot{U}_{AB}}{Z}$

(2)  $i_{ab} \neq \frac{\dot{U}_{AB}}{2Z_L + Z}$

(3)  $i_{ab} \neq \frac{\dot{U}_{AN}}{Z_L + Z/3}$


(4)  $i_A \neq \frac{\dot{U}_{AB}}{2Z_L + Z}$

(5)  $i_A \neq \frac{\dot{U}_{AB}}{Z_L + Z}$


(6)  $i_A = \frac{\dot{U}_{AN}}{Z_L + Z/3}$




1.

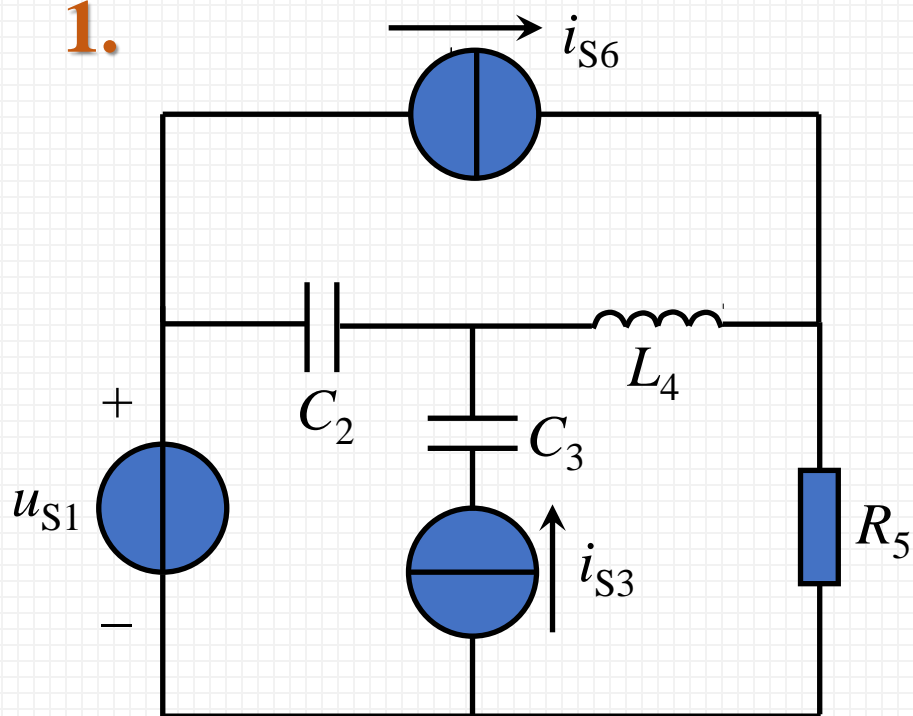

电路如图所示。写出其相量形式的节点方程和回路方程。

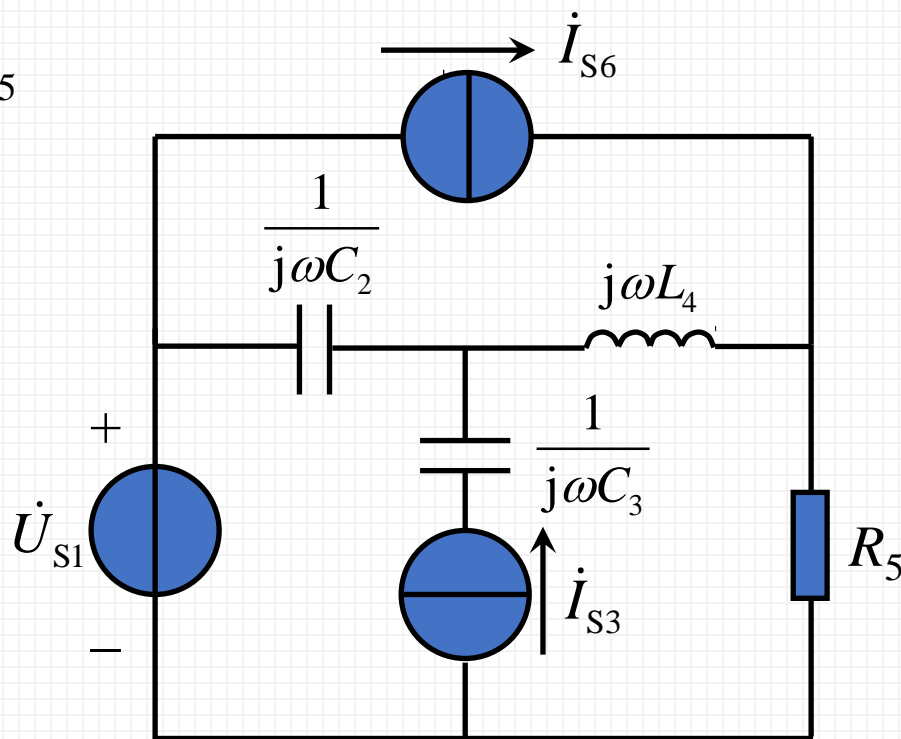

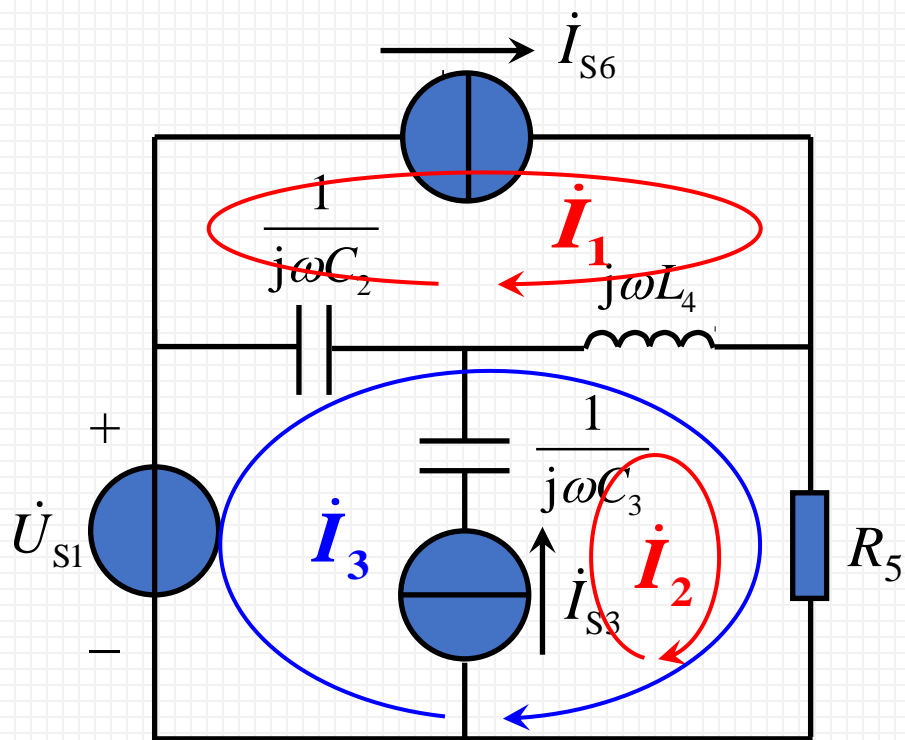


回路法:

$$\dot{I}_1 = \dot{I}_{S6} \quad (1)$$

$$\dot{I}_2 = \dot{I}_{S3} \quad (2)$$


$$\left(\frac{1}{j\omega C_2} + j\omega L_4 + R_5\right) \dot{I}_3 - \left(\frac{1}{j\omega C_2} + j\omega L_4\right) \dot{I}_1 + (j\omega L_4 + R_5) \dot{I}_2 = \dot{U}_{S1} \quad (3)$$

节点法:

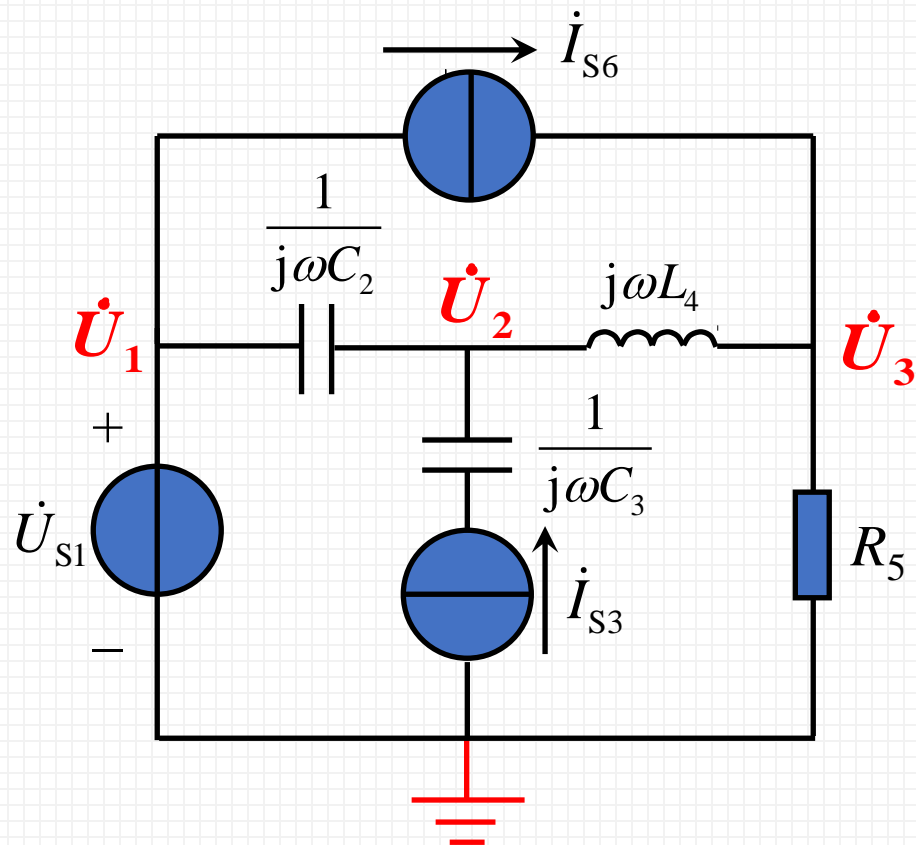


$$\begin{cases} \dot{U}_1 = \dot{U}_{S1} \\ -j\omega C_2 \dot{U}_1 + (j\omega C_2 + \frac{1}{j\omega L_4}) \dot{U}_2 - \frac{1}{j\omega L_4} \dot{U}_3 = \dot{I}_{S3} \\ -\frac{1}{j\omega L_4} \dot{U}_2 + (\frac{1}{j\omega L_4} + \frac{1}{R_5}) \dot{U}_3 = \dot{I}_{S6} \end{cases}$$

2.

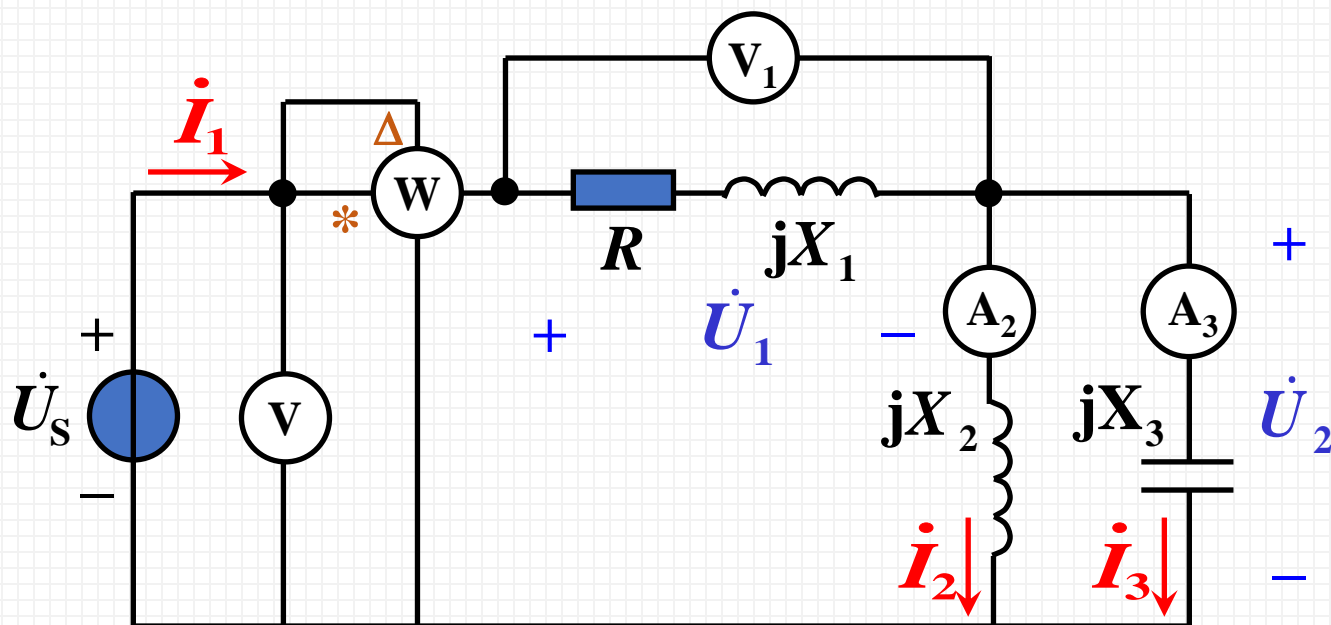

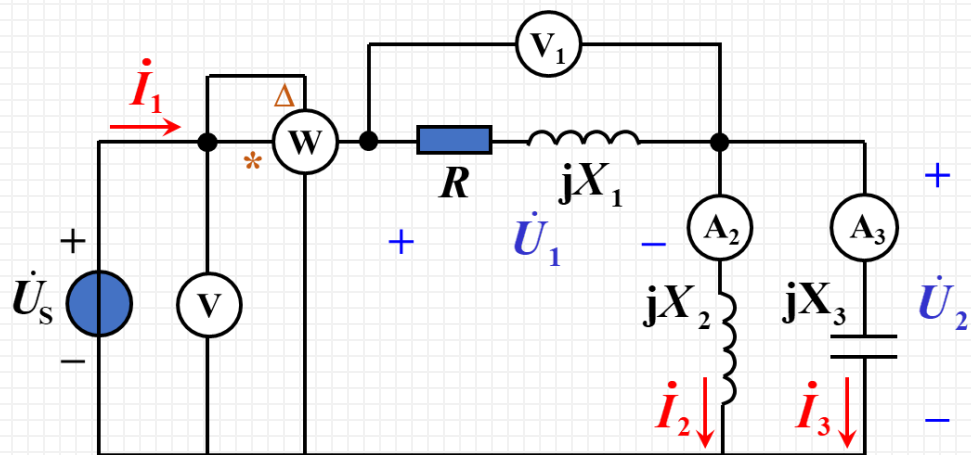电路如图所示。电压表 V 的读数是 220V,  $V_1$  的读数是  $100\sqrt{2}$  V,  $A_2$  的读数是 30A,  $A_3$  的读数是 20A, 功率表的读数是 1000W (有功功率)。  
求参数  $R$ 、 $X_1$ 、 $X_2$  和  $X_3$ 。





设:  $\dot{U}_2 = U_2 \angle 0^\circ \text{ V}$

那么:  $\dot{I}_2 = -j30 \text{ A}$

$\dot{I}_3 = j20 \text{ A}$

$\dot{I}_1 = \dot{I}_2 + \dot{I}_3 = -j10 \text{ A}$

$P = I_1^2 R$

$R = P / I_1^2 = 1000 / 10^2 = 10 \Omega$

设:  $Z_1 = R + jX_1 = |Z_1| \angle \varphi_1$  则  $|Z_1| = \frac{U_1}{I_1} = \frac{100\sqrt{2}}{10} = 10\sqrt{2} \Omega$

$X_1 = \sqrt{|Z_1|^2 - R^2} = \sqrt{(10\sqrt{2})^2 - 10^2} = 10 \Omega$


$\varphi_1 = \arctg \frac{X_1}{R} = 45^\circ$

$\therefore \dot{I}_1 = -j10 = 10 \angle -90^\circ \text{ A} \quad \therefore \dot{U}_1 = 100\sqrt{2} \angle -45^\circ \text{ V}$

$\dot{U}_s = \dot{U}_1 + \dot{U}_2 = 100 - j100 + U_2 = 100 + U_2 - j100$

$U_s^2 = (100 + U_2)^2 + 100^2, \quad U_2 = \sqrt{220^2 - 100^2} - 100 = 96 \text{ V}$

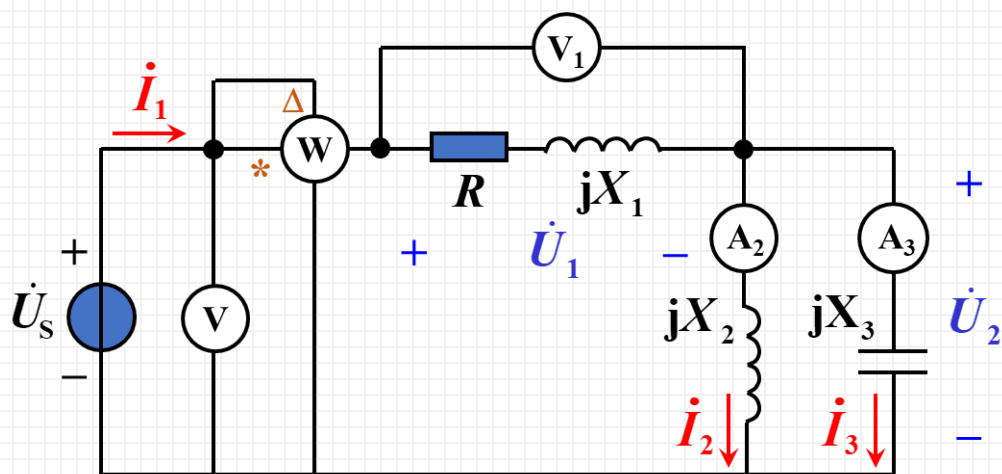$X_2 = U_2 / I_2 = 96 / 30 = 3.2 \Omega, \quad X_3 = -U_2 / I_3 = -96 / 20 = -4.8 \Omega$




$U_2$  也可以用相量图求出.

$$\dot{U}_S = \dot{U}_1 + \dot{U}_2$$

$$\dot{U}_1 = \dot{U}_R + \dot{U}_{X1}$$

$$\dot{I}_1 = \dot{I}_2 + \dot{I}_3$$

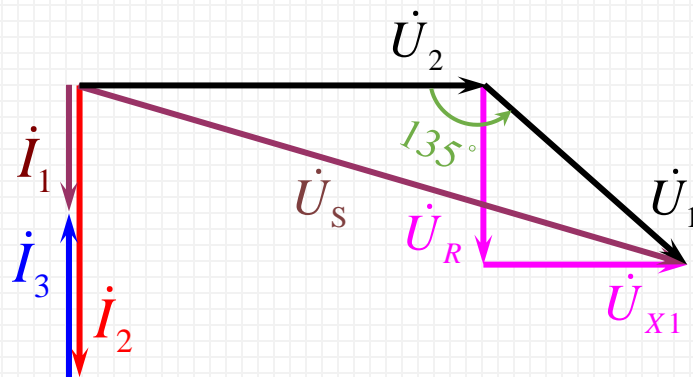


$$U_S^2 = U_2^2 + U_1^2 - 2U_1U_2 \cos 135^\circ$$

$$U_2^2 - 2 \times 100\sqrt{2} \times \left(-\frac{\sqrt{2}}{2}\right)U_2 + (100\sqrt{2})^2 - 220^2 = 0$$

$$U_2^2 + 200U_2 - 28400 = 0, \quad U_2 = 96\text{V} \quad (\text{忽略负值})$$

## 交流电路最大功率传输

讨论正弦电流电路中负载获得最大功率 $P_{\max}$ 的条件。

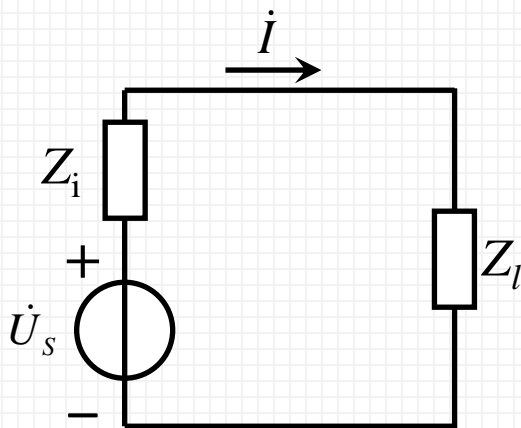

$$Z_i = R_i + jX_i, \quad Z_l = R_l + jX_l$$

$$\dot{I} = \frac{\dot{U}_s}{Z_i + Z_l}, \quad I = \frac{U_s}{\sqrt{(R_i + R_l)^2 + (X_i + X_l)^2}}$$

$Z_l = R_l + jX_l$  可任意改变时

$$Z_l = Z_i^*, \quad \text{即} \quad \begin{cases} R_l = R_i \\ X_l = -X_i \end{cases} \quad P_{\max} = \frac{U_s^2}{4R_i}$$

(2) 若  $Z_l = R_l + jX_l$  只允许  $X_l$  改变

此时获得最大功率的条件  $X_i + X_l = 0$ , 即  $X_l = -X_i$ 。

最大功率为 
$$P_{\max} = \frac{R_l U_S^2}{(R_i + R_l)^2}$$

(3) 若  $Z_l = R_l + jX_l = |Z_l| \angle \phi$ ,  $R_l$ 、 $X_l$  均可改变, 但  $X_l / R_l$  不变



(即  $|Z_l|$  可变,  $\phi$  不变)

模匹配

此时获得最大功率的条件  $|Z_l| = |Z_i|$ 。

最大功率为 
$$P_{\max} = \frac{\cos \phi U_S^2}{2 |Z_i| + 2(R_i \cos \phi + X_i \sin \phi)}$$

3.  $R_L$  取值为多大时获得最大功率？最大功率是多少？

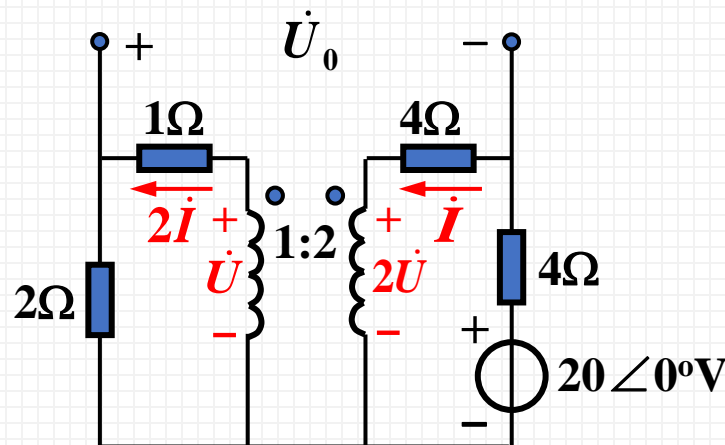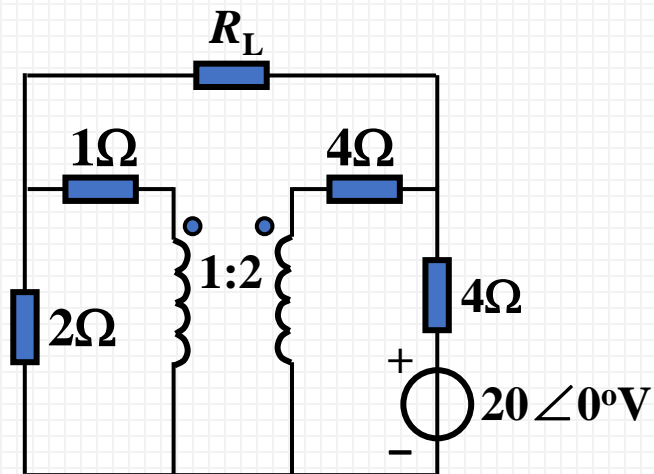

解法：戴维南定理 + 理想变压器

求开路电压

左：  $\dot{U} = 3 \times 2\dot{I}$

右：  $20\angle 0^\circ = 8\dot{I} + 2\dot{U}$



$$\dot{U} = 6\angle 0^\circ$$


$$\dot{I} = 1\angle 0^\circ$$



$$\dot{U}_0 = 2 \times 2\dot{I} - 20\angle 0^\circ + 4\dot{I} = 12\angle 180^\circ \text{ V}$$

求开路电压

法二：

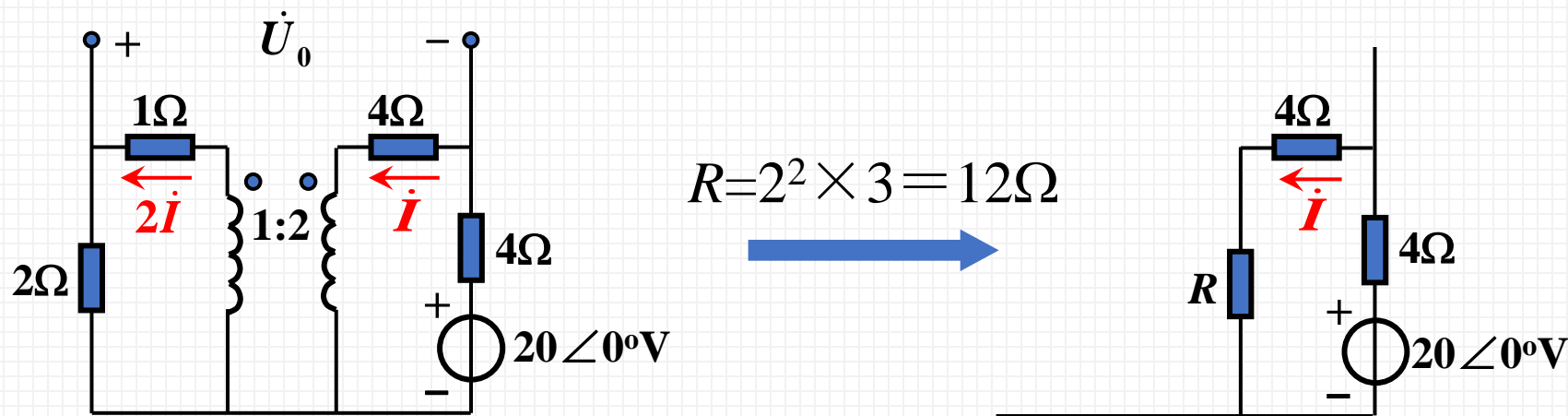


$$\dot{I} = 20\angle 0^\circ / (R + 4 + 4) = 1\angle 0^\circ \text{ A}$$

$$\dot{U}_0 = 2 \times 2\dot{I} - 20\angle 0^\circ + 4\dot{I} = 12\angle 180^\circ \text{ V}$$

并不简便

## 加压求流求内阻

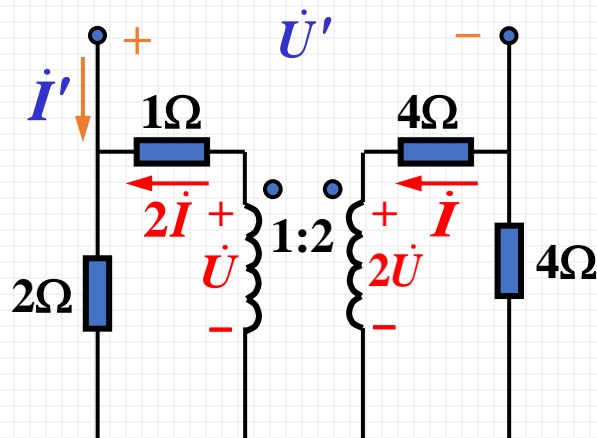


$$\begin{cases} \dot{U} = 2\dot{I} + 2(2\dot{I} + \dot{I}') \\ 4\dot{I} + 2\dot{U} + 4(\dot{I} + \dot{I}') = 0 \\ \dot{U}' = 2(2\dot{I} + \dot{I}') + 4(\dot{I} + \dot{I}') \end{cases} \quad \Rightarrow \quad \begin{aligned} \dot{U}' &= 2.8\dot{I}' \\ R &= 2.8\Omega \end{aligned}$$

则  $R_L = 2.8\Omega$  时获得最大功率.

最大功率  $P = 12^2 / (4 \times 2.8) = 12.9\text{W}$


4. 求图示电路的谐振频率以及在谐振时的入端阻抗 ( $0 < k < 1$ )

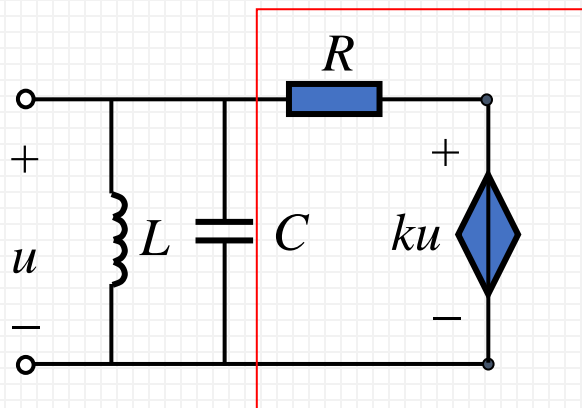

$$R_{\text{等}} = \frac{u}{(1-k)u/R} = \frac{R}{1-k}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$Z(\omega_0) = \frac{R}{1-k}$$

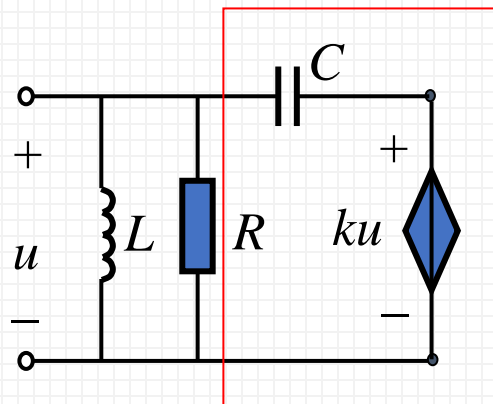


$$Z_{\text{等}} = \frac{\dot{U}}{(1-k)\dot{U}j\omega C} = \frac{1}{(1-k)j\omega C}$$


$$\omega_0 = \frac{1}{\sqrt{LC(1-k)}}$$

$$Z(\omega_0) = R$$



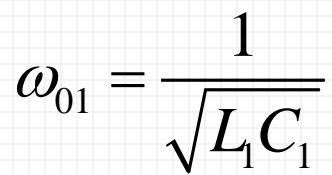
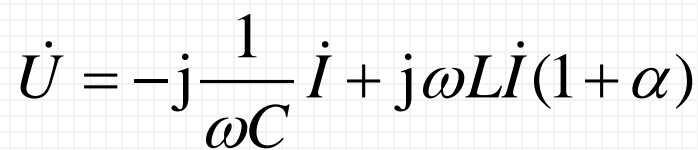
$$\omega_{02} = \frac{1}{\sqrt{L_1 \frac{C_1 C_2}{C_1 + C_2}}}$$




$$Z = \frac{\dot{U}}{\dot{I}} = -j\frac{1}{\omega C} + j(1 + \alpha)\omega L$$

$$\omega_0 = \frac{1}{\sqrt{(1+\alpha)LC}}$$

5. 电路如图所示.  $u_s(t)=\sin t$  V,  $L_1=L_2=1$  H,  $C_1=C_2=1$  F,  $R=1\Omega$ .

求电压表和电流表的读数 (rms).

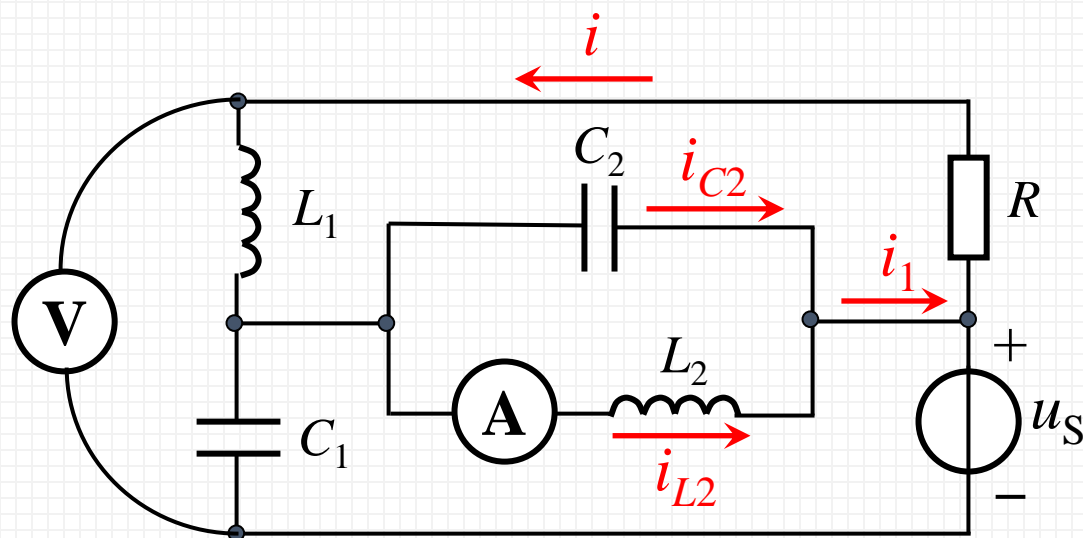

解: 设  $\dot{U}_s = \frac{1}{\sqrt{2}} \angle 0^\circ$  V

$= 0.707 \angle 0^\circ$  V

$\omega L_2 = \frac{1}{\omega C_2} = 1\Omega$


(并联谐振)  $\dot{I}_1 = 0$

$\omega L_1 = \frac{1}{\omega C_1} = 1\Omega$  (串联谐振),  $\textcircled{\text{V}} = 0$   $\dot{I} = \frac{\dot{U}_s}{R} = \frac{0.707 \angle 0^\circ}{1} = 0.707 \angle 0^\circ$  A


$\dot{I}_{L2} = \frac{\frac{1}{j\omega C_1} \dot{I} - \dot{U}_s}{j\omega L_2} = \frac{-j0.707 - 0.707}{j1} = -0.707 + j0.707 = 1.00 \angle 135^\circ$  A

$\textcircled{\text{A}} = 1\text{A}$

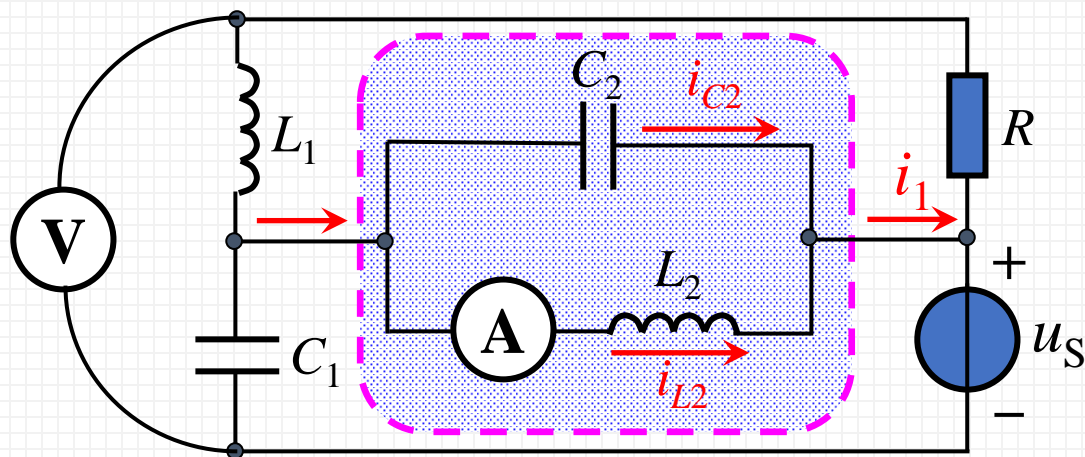
将发生并联谐振的电路看成一个二端网络 (或一条广义的支路), 则流进或流出端口的电流 (或通过该广义支路的电流) 为零, 但网络内部的各个支路的电流 **并不一定为零**。



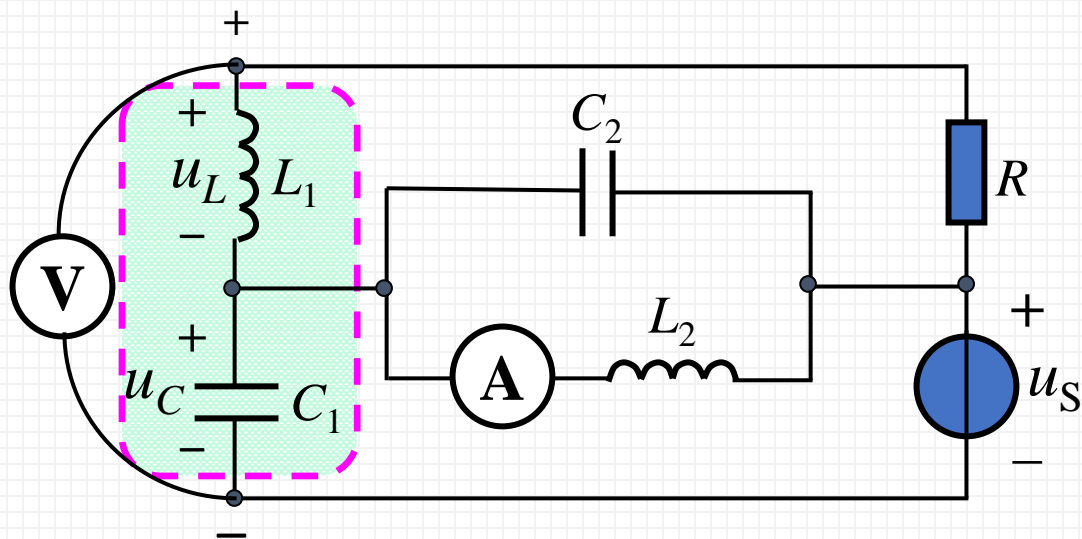
将发生串联谐振的电路看成一个二端网络 ( 或一条广义的支路), 则两个端钮之间的电压 ( 或广义支路两端的电压) 为零, 但网络内部的各个支路上的电压**并不一定为零**。



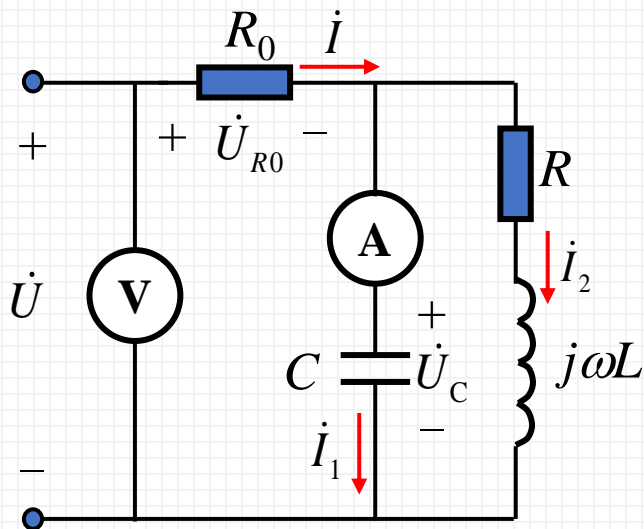6.  $\omega = 1000 \text{ rad/s}$  时, 电路发生谐振。  $R_0 = 25 \Omega$ ,  $C = 16 \mu\text{F}$ , 电压表的读数是  $100 \text{ V}$ , 电流表的读数是  $1.2 \text{ A}$ , 求  $R$  和  $L$ .



解: 相量图

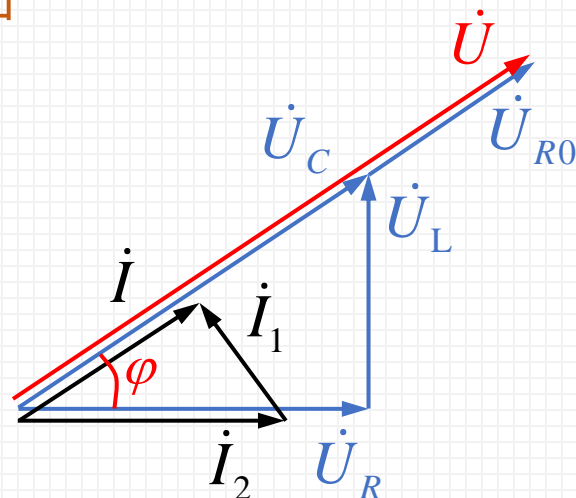

$$I_1 = 1.2 \text{ A}$$

$$U_C = 1.2 / (1000 \times 1.6 \times 10^{-6}) = 75 \text{ V}$$

谐振时:

$$U_{R0} = 25 \text{ V} \quad I = 1 \text{ A}$$

$$I_2 = \sqrt{I_1^2 + I^2} = 1.562 \text{ A}$$

$$\phi = \arctan(I_1 / I) = 50.2^\circ$$

$$|Z| = U_C / I_2 = 75 / 1.562 = 48.01 \Omega$$

$$R = 48.01 \cos 50.2^\circ = 30.7 \Omega$$

$$L = 48.01 \sin 50.2^\circ / 1000 = 36.9 \text{ mH}$$

## 解二

设  $\dot{U} = 100\angle 0^\circ \text{ V}$


分析可知  $u$ 、 $i$ 、 $u_2$  同相，则  $i_1$  领先  $u_2$  90度

$$\dot{I}_1 = j1.2 \text{ A}$$

$$\dot{U}_2 = \dot{I}_1 * \frac{1}{j\omega C} = 75\angle 0^\circ \text{ V}$$

$$\dot{I} = \frac{\dot{U} - \dot{U}_2}{R_0} = 1 \text{ A}$$
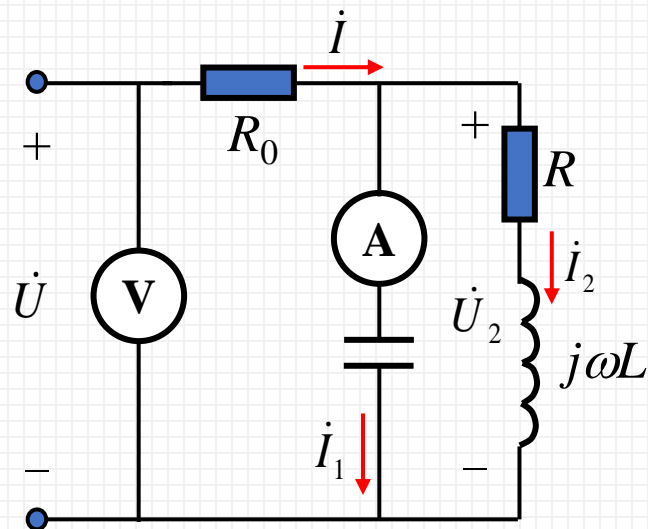
$$\dot{I}_2 = \dot{I} - \dot{I}_1 = 1 - j1.2 = 1.562\angle 50.2^\circ \text{ A}$$



由于谐振，无功在电感与电容间交换，则

$$Q_L = I_2^2 \omega L \quad Q_C = -I_1^2 \frac{1}{\omega C}$$

$$I_1^2 \frac{1}{\omega C} = I_2^2 \omega L$$

$$\Rightarrow L = \frac{I_1^2}{\omega^2 C I_2^2} = 0.0369 \text{ H}$$

$$R = \sqrt{\left(\frac{U_2}{I_2}\right)^2 - (\omega L)^2} = \sqrt{\left(\frac{75}{1.562}\right)^2 - (39.6)^2} = 30.7 \Omega$$

设  $\dot{U} = 100\angle 0^\circ \text{V}$

$$I_C = j1.2A \quad jX_C = \frac{1}{j\omega C} = \frac{1}{j \times 1000 \times 16 \times 10^{-6}} = -j62.5\Omega$$

$$\dot{U}_C = I_C jX_C = 75\text{V} \quad \dot{U}_{R0} = \dot{U} - \dot{U}_C = 100 - 75 = 25\text{V}$$

$$I = \frac{\dot{U}_{R0}}{R_0} = \frac{25\angle 0^\circ}{25} = 1\angle 0^\circ \text{ A}$$

所以 $R$ ,  $L$ ,  $C$  并联支路等效为一个  $\frac{\dot{U}_C}{\dot{I}} = 75\Omega$  的电阻。即:


$$\frac{\frac{1}{j\omega C} \times (R + j\omega L)}{\frac{1}{j\omega C} + (R + j\omega L)} = 75\Omega$$

$$Z = 30.7 + j36.9\Omega$$

$$R = 30.7\Omega$$



$$\omega L = 36.9\Omega$$

$$L = 36.9\text{mH}$$

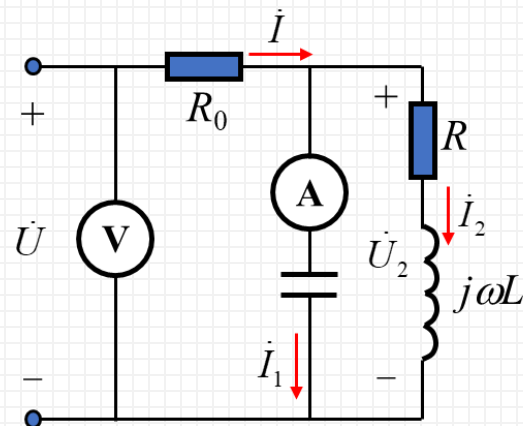


则有:  $\frac{-j62.5 \times Z}{-j62.5 + Z} = 75$

## 7. W的读数有何物理意义

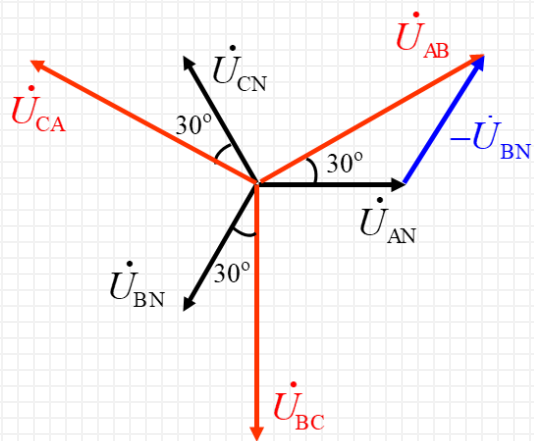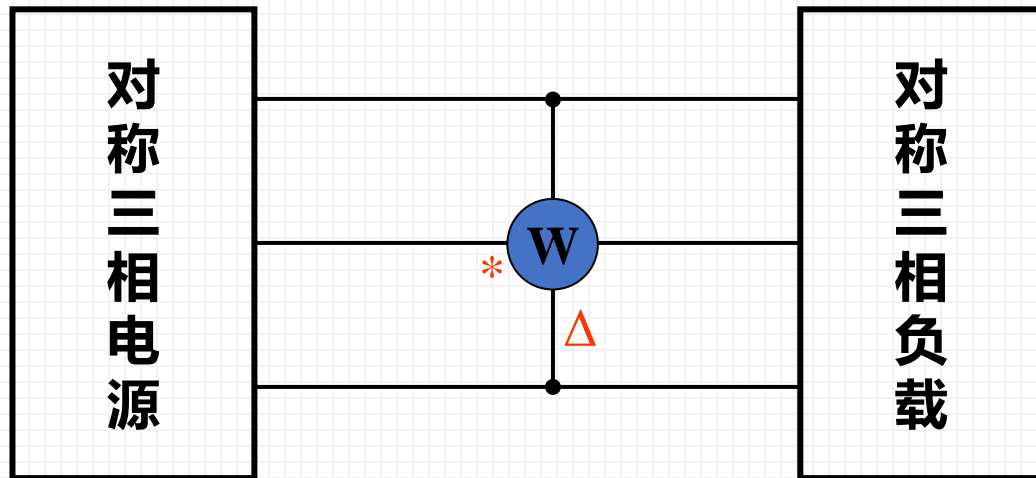

设  $\dot{U}_{AN} = U_P \angle 0^\circ$

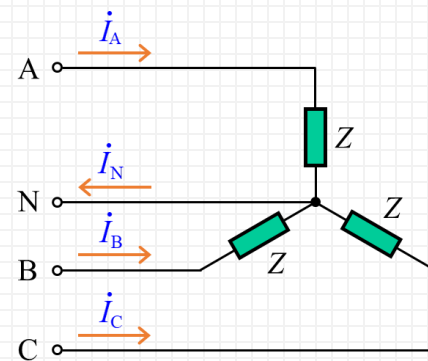
$$\begin{aligned} [W] &= U_{CA} I_B \cos(\phi_{u_{CA}} - \phi_{i_B}) \\ &= \sqrt{3} U_P I_P \cos((150^\circ) - (-120^\circ - \phi_P)) \\ &= \sqrt{3} U_P I_P \cos(270^\circ + \phi_P) \\ &= \sqrt{3} U_P I_P \sin \phi_P \end{aligned}$$




测量对称三相负载吸收的无功功率  $\times \sqrt{3}$



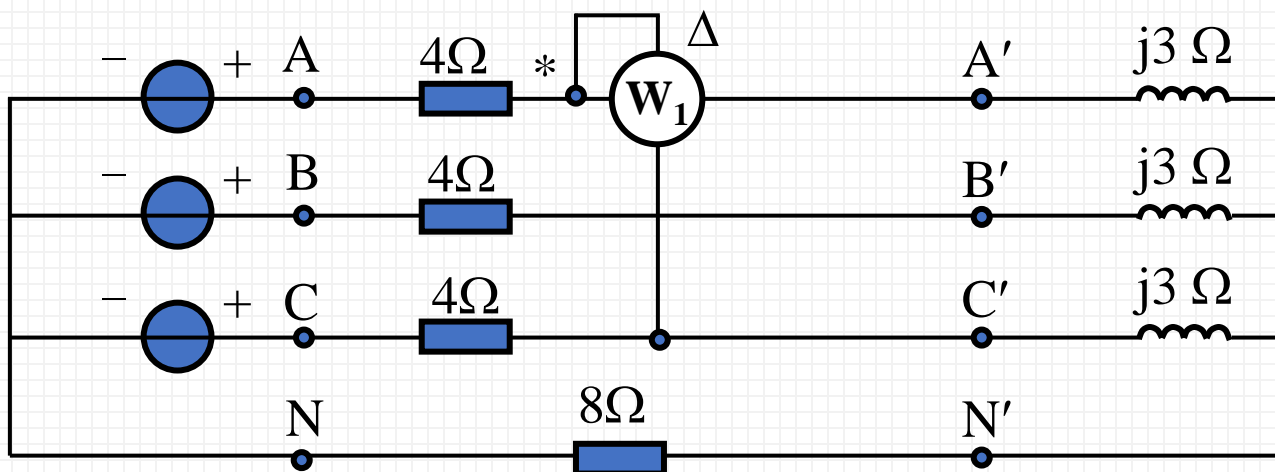8. 平衡三相电路的相电压是 220V。求: (1)线电流和通过中线的电流; (2) 求功率表的读数; (3)电源发出的有功功率和无功功率; (4)能用两表法测量负载吸收的功率吗? 如果能, 画出另一块表, 求读数。



**解：(1) 抽单相：**

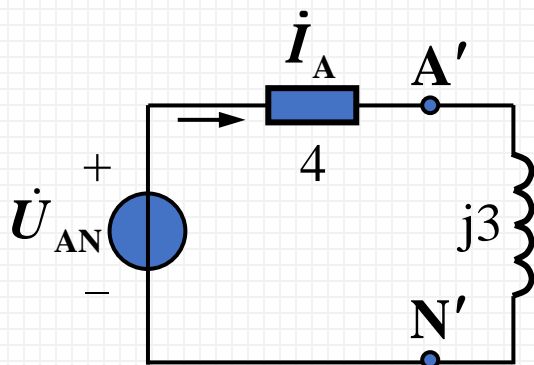


$$\dot{U}_{AN} = 220 \angle 0^\circ \text{ V}$$

$$I_A = \frac{220 \angle 0^\circ}{4 + j3} = 44 \angle -36.9^\circ \text{ A}$$

$$I_I = 44\text{A} \quad I_N = 0$$
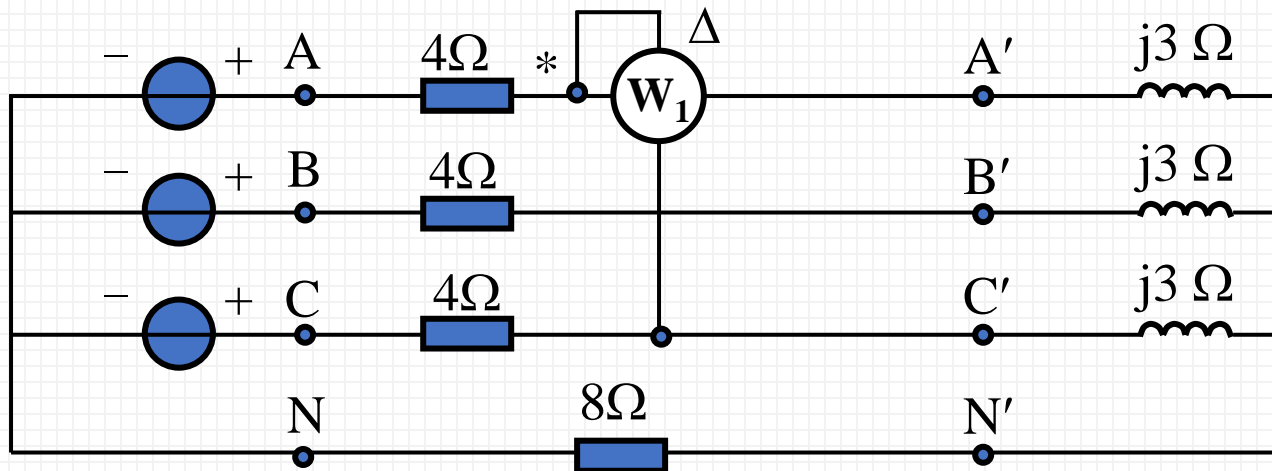
## (2) 求功率表的读数


$$\dot{I}_A = 44 \angle -36.9^\circ \text{ A}$$



$$\dot{U}_{A'N} = j3\dot{I}_A = 132 \angle 53.1^\circ \text{ V}$$

$$\dot{U}_{A'B'} = \sqrt{3} 132 \angle (30^\circ + 53.1^\circ) = \sqrt{3} 132 \angle 83.1^\circ \text{ V}$$
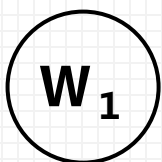
$$\dot{U}_{A'C'} = -\dot{U}_{C'A'} = -\sqrt{3} 132 \angle (120^\circ + 83.1^\circ) = \sqrt{3} 132 \angle 23.1^\circ \text{ V}$$



$$\begin{aligned} & U_{A'C'} I_A \cos[23.1^\circ - (-36.9^\circ)] \\ &= \sqrt{3} 132 \times 44 \cos 60^\circ = 5029 \text{ W} \end{aligned}$$

(3) 电源发出的功率:

$$\dot{U}_{AN} = 220 \angle 0^\circ \text{ V}$$

$$\dot{I}_A = 44 \angle -36.9^\circ \text{ A}$$

$$P = 3U_p I_p \cos \phi_p = 3 \times 220 \times 44 \cos 36.9^\circ = 23.2 \text{ kW}$$

OR  $P = \sqrt{3}U_l I_l \cos \phi_p = \sqrt{3} \times \sqrt{3} \times 220 \times 44 \cos 36.9^\circ = 23.2 \text{ kW}$


$$Q = 3U_p I_p \sin \phi_p = 3 \times 220 \times 44 \sin 36.9^\circ = 17.4 \text{ kvar}$$

另一种求法:

$$P = 3I_l^2 R = 3 \times 44^2 \times 4 = 23.2 \text{ kW}$$

$$Q = 3I_l^2 X = 3 \times 44^2 \times 3 = 17.4 \text{ kvar}$$

#### (4) 可以用两表法测负载功率

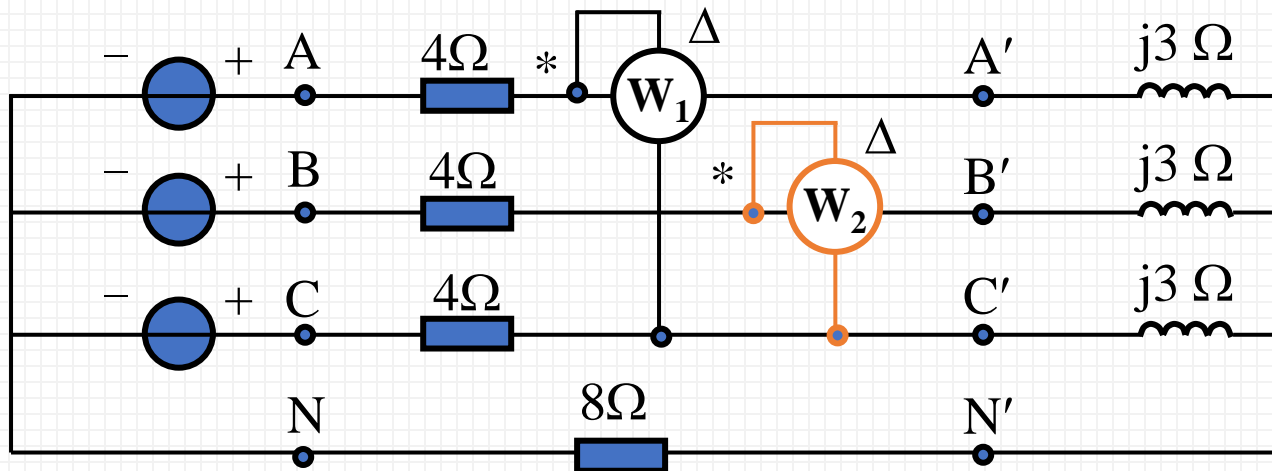


$$\dot{U}_{A'B'} = \sqrt{3} \, 132 \angle 83.1^\circ \text{ V} \quad \dot{I}_A = 44 \angle -36.9^\circ \text{ A}$$

$$\dot{U}_{B'C'} = \sqrt{3} \, 132 \angle -36.9^\circ \text{ V} \quad \dot{I}_B = 44 \angle -156.9^\circ \text{ A}$$

$$\begin{aligned} & \textcircled{W_2} \quad U_{B'C'} I_B \cos[(-36.9^\circ) - (-156.9^\circ)] \\ & = \sqrt{3} 132 \times 44 \cos 120^\circ = -5029 \text{ W} \end{aligned}$$

$$\textcircled{W_1} = 5029 \text{ W}$$

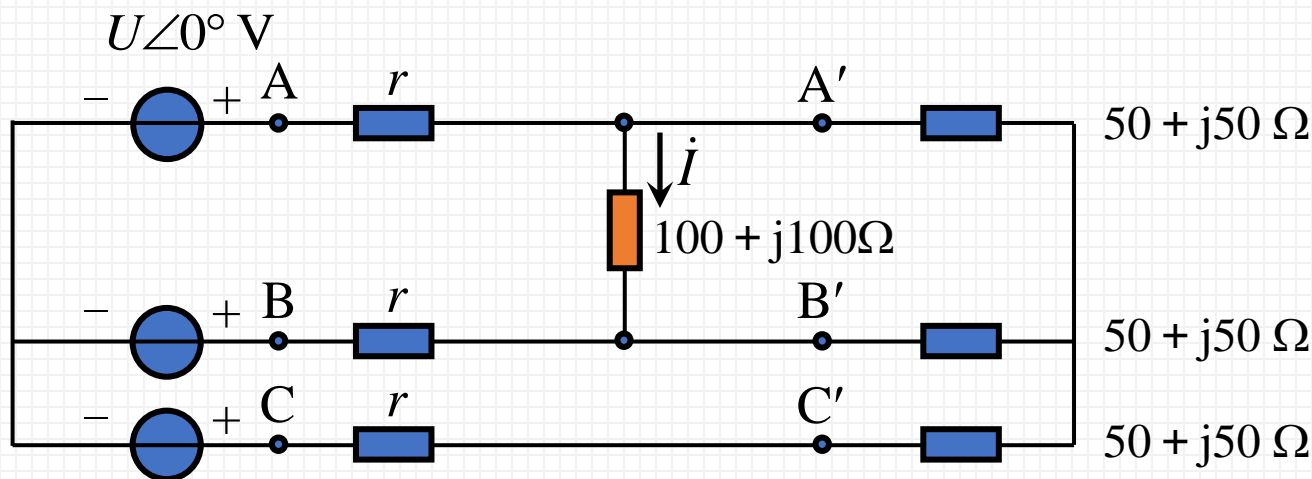9. 电源三相对称,  $r$  分别为0和10 $\Omega$ 时求  $\dot{i}$ 。



解: (1)  $r = 0$        $\dot{i} = \frac{\dot{U}_{AB}}{100 + j100} = 0.0122U \angle -15^\circ$

(2)  $r = 10 \Omega$       戴维南等效

开路电压: 抽单相       $\dot{U}_{oc} = 1.56U \angle 35.2^\circ$

等效内阻抗: 交流电桥平衡       $Z_{eq} = 18.03 + j1.64\Omega$

$$\dot{i} = \frac{\dot{U}_{oc}}{Z_{eq} + 100 + j100} = 0.01U \angle -5.53^\circ$$